



**D1, D2, D3, D4 = 1N5408 (could be replaced with similar diode for current  $\geq 3A$ )**

**D5, D6, D9, D10 = 1N4148 diode**

**D7, D8 = 5,1V zener diode**

**D11 = 1N4001 (could be replaced with 1N4002..1N4007 or similar 1A diode)**

**D12 = LED**

**Q1 = 9014 (could be replaced with BC547, BC548 or other similar NPN transistor)**

**Q2 = 2SD882 (can be 2N2219, BC141, BC286, or BD137 or BD139 are even better)**

**Q3 = 9015 (can be BC557, BC558, BC327 or other similar PNP transistor)**

**Q4 = 2SD1047 have to be mounted on heat sink (instead original transistor could be used TIP3055, 2N3055 or other similar NPN transistor )**

**U1, U2, U3 = TL081 operational amplifier**

**R1 = 2k2 (original is 1W, but it is better to be replaced by 2W resistor)**

**R2 = 82 Ohm (original is 0.25W, but it is better to be replaced by 0.5W resistor)**

**R3 = 220 Ohm (original is 0.25W, but it is better to be replaced by 0.5W resistor)**

**R4 = 4k7 – 0.25 W**

**R5, R6, R13, R20, R21 = 10k – 0.25 W**

**R7 = 0.47 Ohm - 5W (it is good to be soldered 3-4mm above PCB)**

**R8, R11 = 27k – 0.25 W**

**R9, R19 = 2k2 – 0.25 W**

**R10 = 270k – 0.25 W**

**R12, R18 = 56k – 0.25 W**

**R14 = 1k5 – 0.25 W**

**R15, R16 = 1k – 0.25 W**

**R17 = 33 Ohm – 0.25 W**

**R22 = 3k9 – 0.25 W**

**RV1 = 100k (linear trimmer potentiometer)**

**P1, P2 = 10k (linear potentiometer)**

**C1 = 3300  $\mu F$  / 50V (electrolytic capacitor)**

**C2, C3 = 47  $\mu F$  / 50V (electrolytic capacitor)**

**C4 = 100nF (polyester capacitor)**

**C5 = 220nF (polyester capacitor)**

**C6, C9 = 100pF (ceramic capacitor)**

**C7 = 10  $\mu F$  / 50V (electrolytic capacitor)**

**C8 = 330pF (ceramic capacitor)**

**LM7812 – fixed voltage regulator 12V (have to be mounted on heat sink)**

